

**CSC258 Computer Organization 2015 fall**  
**Assignment 1 due Thu.Oct.8 at 6pm in BA2220**


1[10] Prove that the following three expressions are equivalent.

**if  $x$  then  $y$  else  $z$**

**if  $y$  then  $z \vee x$  else  $z > x$**

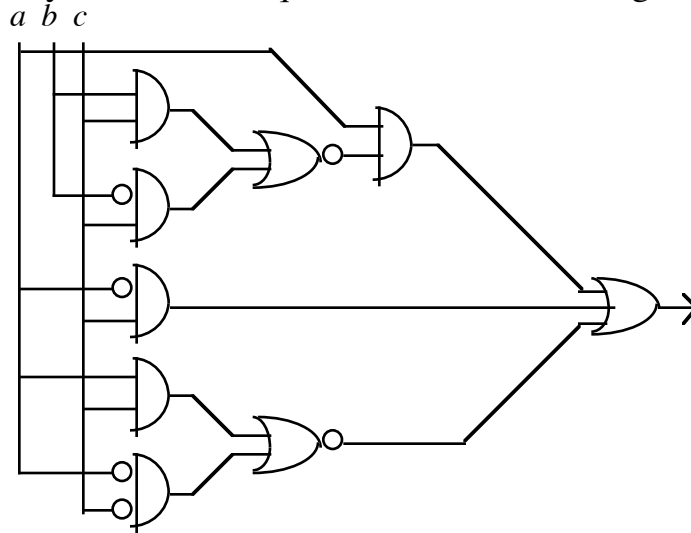**if  $z$  then  $x \leq y$  else  $x \wedge y$**

2[10] Find the simplest circuit you can that's equivalent to the following circuit.



3[5] Prove that  $\triangle$  is complete.

4[10] Prove that  $\neq$  is not complete. Hint: Find a systematic way to show all functions that can be created from  $\neq$ , and show some function that is not created. Or find a property of all functions that can be created from  $\neq$ , and show some function that does not have that property.

5[15] Design a circuit whose 4 bits of input represent a number  $x$  from 0 to 15, and whose bits of output represent two numbers  $y$  and  $z$  such that  $x = y \times z$  and  $y \geq z$ , and of all pairs whose product is  $x$ , the pair  $y$  and  $z$  has the smallest sum.